

**CSE206 (Digital Logic Design Sessional)**

**Experiment No. 04**

**Name of the Experiment**

Comparator, adder / subtractor

<b>Group no.</b>	<b>01</b>
<b>Group Members</b>	<b>1805061, 1805062, 1805063, 1805064, 1805065</b>
<b>Section</b>	<b>B1</b>
<b>Department</b>	<b>CSE</b>
<b>Date of Submission</b>	<b>03.04.2021</b>

## Problem No. 01

### Problem specification:

Design using basic gates, a 2-bit comparator to compare 2-bit numbers X and Y. The circuit should provide 3 output lines to indicate  $X > Y$ ,  $X = Y$  and  $X < Y$ .

### Required instruments:

No.	Name of the Instrument	Quantity
1	IC - Hex 1-input Inverter gate (74x04)	1 piece
2	IC- Quad 2-input AND gate (74x08)	2 pieces
3	IC- Quad 2-input OR gate (74x32)	1 piece
4	IC- Quad 2-input XOR gate (74x86)	1 piece
5	Input pin	4 pieces
6	Output pin	3pieces
7	Wires	A lot
8	Software Logisim	

### Truth Table:

Here  $A_1$ ,  $A_0$ ,  $B_1$ ,  $B_0$  are the input pins and L, E, G are the output pins. L is on when  $A < B$ , E is on when  $A = B$  and G is on when  $A > B$ . The truth table is shown below:

$A_1$	$A_0$	$B_1$	$B_0$	L	E	G
0	0	0	0	0	1	0
0	0	0	1	1	0	0
0	0	1	0	1	0	0
0	0	1	1	1	0	0
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	1	0	0
0	1	1	1	1	0	0
1	0	0	0	0	0	1
1	0	0	1	0	0	1
1	0	1	0	0	1	0
1	0	1	1	1	0	0
1	1	0	0	0	0	1
1	1	0	1	0	0	1
1	1	1	0	0	0	1
1	1	1	1	0	1	0

**Simplification of the Equation:**

From the truth table we can derive the equation of L, E, and G.

Now,


$$\begin{aligned} L &= A_1'A_0'B_1'B_0 + A_1'A_0'B_1B_0' + A_1'A_0'B_1B_0 + A_1'A_0B_1B_0' + A_1'A_0B_1B_0 + A_1A_0'B_1B_0 \\ &= A_1'A_0'B_1B_0' + A_1'A_0'B_1B_0 + A_1'A_0B_1B_0' + A_1'A_0B_1B_0 + A_1'A_0'B_1'B_0 + A_1A_0'B_1B_0 \\ &= A_1'B_1(A_0'B_0' + A_0'B_0 + A_0B_0' + A_0B_0) + (A_1'B_1' + A_1B_1)A_0'B_0 \\ &= A_1'B_1(A_0'(B_0' + B_0) + A_0(B_0' + B_0)) + (A_1 \oplus B_1)'A_0'B_0 \quad [X'Y' + XY = (X \oplus Y)'] \\ &= A_1'B_1(A_0' + A_0) + (A_1 \oplus B_1)'A_0'B_0 \quad [X' + X = 1 \text{ and } X.1 = X] \\ &= A_1'B_1 + (A_1 \oplus B_1)'A_0'B_0 \end{aligned}$$

$$\begin{aligned} E &= A_1'A_0'B_1'B_0' + A_1'A_0B_1'B_0 + A_1A_0'B_1B_0' + A_1A_0B_1B_0 \\ &= A_1'B_1'(A_0'B_0' + A_0B_0) + A_1B_1(A_0'B_0' + A_0B_0) \\ &= (A_1'B_1' + A_1B_1)(A_0'B_0' + A_0B_0) \\ &= (A_1 \oplus B_1)'(A_0 \oplus B_0)' \quad [X'Y' + XY = (X \oplus Y)'] \end{aligned}$$

$$\begin{aligned} G &= A_1'A_0B_1'B_0' + A_1A_0'B_1'B_0' + A_1A_0'B_1'B_0 + A_1A_0B_1'B_0' + A_1A_0B_1'B_0 + A_1A_0B_1B_0' \\ &= A_1A_0'B_1'B_0' + A_1A_0'B_1'B_0 + A_1A_0B_1'B_0' + A_1A_0B_1'B_0 + A_1'A_0B_1'B_0' + A_1A_0B_1B_0' \\ &= A_1B_1'(A_0'B_0' + A_0'B_0 + A_0B_0' + A_0B_0) + (A_1'B_1' + A_1B_1)A_0B_0' \\ &= A_1B_1'(A_0'(B_0' + B_0) + A_0(B_0' + B_0)) + (A_1 \oplus B_1)'A_0B_0' \quad [X'Y' + XY = (X \oplus Y)'] \\ &= A_1B_1'(A_0' + A_0) + (A_1 \oplus B_1)'A_0B_0' \quad [X' + X = 1 \text{ and } X.1 = X] \\ &= A_1B_1' + (A_1 \oplus B_1)'A_0B_0' \end{aligned}$$

### Circuit Diagram:

The circuit diagram is shown below-

 

### Observation:

We can make some observations from the truth table and the simplified equations and can derive equations for a n-bit comparator.

- E Function:

From the truth table we can see that, output pin E will be on if  $A_i = B_i$ , where  $i=0, 1, \dots, n-1$ .

Two bits  $A_i$  and  $B_i$  are equal if,  $x_i = (A_i \odot B_i) = (A_i \oplus B_i)'$  holds.

So, for n-bit comparator,  $E = x_0 x_1 \dots x_{n-1}$ , where  $x_i = (A_i \oplus B_i)'$ .

- L Function:

From the truth table we can see that, output pin L will be on if

- $A_{n-1} < B_{n-1}$
- $A_{n-1} = B_{n-1}$  and  $A_{n-2} < B_{n-2}$
- $A_{n-1} = B_{n-1}$  and  $A_{n-2} = B_{n-2}$  and  $A_{n-3} < B_{n-3}$  and so on.

So, for n-bit comparator,  $L = A_{n-1}'B_{n-1} + x_{n-1} A_{n-2}'B_{n-2} + \dots + x_{n-1}x_{n-2}\dots x_1 A_0'B_0$ ,

where  $x_i = (A_i \oplus B_i)'$ .

- G Function:

From the truth table we can see that, output pin L will be on if

- $A_{n-1} > B_{n-1}$
- $A_{n-1} = B_{n-1}$  and  $A_{n-2} > B_{n-2}$
- $A_{n-1} = B_{n-1}$  and  $A_{n-2} = B_{n-2}$  and  $A_{n-3} > B_{n-3}$  and so on.

So, for n-bit comparator,  $L = A_{n-1}B_{n-1}' + x_{n-1} A_{n-2}B_{n-2}' + \dots + x_{n-1}x_{n-2}\dots x_1 A_0B_0'$ ,

where  $x_i = (A_i \oplus B_i)'$ .

## Problem No. 02

### Problem specification:

Design a 1-bit full subtractor circuit using basic logic gates. Inputs are P, Q and R denoting minuend, subtrahend and previous borrow respectively. The outputs are D and B representing the difference and output borrow.

### Required instruments:

No.	Name of the Instrument	Quantity
1	IC - Hex 1-input Inverter gate (74x04)	1 piece
2	IC- Quad 2-input AND gate (74x08)	1 piece
3	IC- Quad 2-input OR gate (74x32)	1 piece
4	IC- Quad 2-input XOR gate (74x86)	1 piece
5	Input pin	3 pieces
6	Output pin	2 pieces
7	Wires	A lot
8	Software Logisim	

### Truth Table:

Here P, Q, R are the input pins and D and Bout is the output pin.

The truth table of the equation of F:

Inputs			Outputs	
Minuend(P)	Subtrahend(Q)	Borrow(R)	D	Bout
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

### Simplification of the Equation:

$$\begin{aligned} D &= P'Q'R + P'QR' + PQ'R' + PQR \\ &= R(P'Q' + PQ) + R'(P'Q + PQ') \\ &= R(P'Q + PQ')' + R'(P'Q + PQ') \\ &= P \oplus Q \oplus R \end{aligned}$$

So, the simplified equation is for D:  $P \oplus Q \oplus R$

And,


$$B(\text{out}) = P'Q'R + P'QR' + P'QR + PQR$$

$$= P'(Q'R + QR') + QR(P + P')$$

$$= P'(Q \oplus R) + QR \quad [\text{since } P + P' = 1]$$

So, the simplified equation is for B(out):  $P'(Q \oplus R) + QR$

### Circuit Diagram:

 

### Observation:

After simplifying the equation, we can see that the function represents  $P \oplus Q \oplus R$

And  $P'(Q \oplus R) + QR$ . Combination of X-OR and AND gates.